

--	--	--	--	--

Time : 2 Hours

DIGITAL ELECTRONICS AND COMPUTERS

Subject Code

V	3	3	1
---	---	---	---

Total No. of Questions : 5

(Printed Pages : 3)

Maximum Marks : 50

INSTRUCTIONS :

- (i) Answer each question on a fresh page.
- (ii) Write the number of the questions and sub-questions clearly.
- (iii) All questions are compulsory.
- (iv) Figures to the right indicate full marks.
- (v) Draw neat diagrams wherever necessary.

1. (a) Fill in the blanks : 2
 - (i) 2's complement of $(100)_2$ is
 - (ii) Binary digits are usually contracted to
- (b) Answer the following :
 - (i) With the help of a neat circuit diagram and truth table explain the working of 2 input RTL NOR gate. 3
 - (ii) Explain the working of logic circuit used to add 3 bits with the help of a neat diagram and truth table. 3
- (c) Answer the following :
 - State and prove De-Morgan's second theorem. 2
2. (a) Define the following : 2
 - (i) Monostable multivibrator
 - (ii) Super Computer.

- (b) Answer the following :
- (i) Explain the working of a four bit shift register with the help of neat logic circuit diagram. 3
- (ii) Explain any *three* applications of microprocessor. 3
- (c) Answer the following : 2
- What is the difference between edge triggering and level clocking ?
3. (a) Fill in the blanks : 2
- (i) The logic circuit used to add 2 bits is called
- (ii) The diameter of mini floppy is
- (b) Do as directed : 3
- (i) Convert $(64)_8$ to its decimal equivalent.
- (ii) Convert $(2879)_{10}$ to its hexadecimal equivalent.
- (iii) Convert $(8CB)_{16}$ to its decimal equivalent.
- (c) Answer the following in detail : 5
- (i) With the help of a neat circuit diagram explain the working of Transistorised Bistable Multivibrator.
- Or*
- (ii) Explain the working of positive edge triggered J-K flip flop with the help of neat logic diagram.
4. (a) Answer the following in one sentence : 2
- (i) What is the IC number used as a clock generator driver in 8080 A microprocessor ?
- (ii) What is the output of a 2-input X-NOR gate if the two inputs are high ?

- (b) Answer the following : 3
What are impact and non-Impact printers ? State one example of each.
- (c) Answer the following in detail : 5
- (i) Define Modulus of a counter. Explain the working of a counter having modulus 10 with the help of a neat logic circuit diagram.
- Or*
- (ii) Explain the working of a 3-bit synchronous counter with the help of neat logic circuit diagram.
5. (a) Answer the following :
- (i) What are volatile and non-volatile memories ? 2
- (ii) Draw the block diagram of microprocessor. 2
- (iii) Why “A” to “D” and “D” to “A” are necessary in a computer system ? 2
- (iv) Explain briefly magnetic tape as a storage device. 2
- (v) Draw the block diagram of a counter type “A” to “D” Convertor. 2